

# GATE 2018 ph, Question 13 — Detailed Analysis

## Question 13

A 2-to-1 multiplexer selects between inputs  $A_0$  and  $A_1$  using select line  $C$ . The output is  $X = A_0$  when  $C = 0$  and  $X = A_1$  when  $C = 1$ . Which gate-level implementation corresponds to this behavior?

## Short Answer

The canonical implementation is:

$$X = \overline{C}A_0 + CA_1$$

(That is, invert  $C$ ; AND  $\overline{C}$  with  $A_0$ ; AND  $C$  with  $A_1$ ; OR the results.)

## Detailed Analysis and Derivation

### 1. Reasoning from the specification:

- Required behavior:

- If  $C = 0$  then  $X = A_0$ .
- If  $C = 1$  then  $X = A_1$ .

- A standard way to encode a select is:

$$X = (\text{select for } A_0) \cdot A_0 + (\text{select for } A_1) \cdot A_1.$$

Here the select for  $A_0$  is  $\overline{C}$  and for  $A_1$  is  $C$ . Hence:

$$X = \overline{C}A_0 + CA_1.$$

### 2. Check by cases:

$$C = 0 \implies X = \overline{0}A_0 + 0 \cdot A_1 = 1 \cdot A_0 + 0 = A_0,$$

$$C = 1 \implies X = \overline{1}A_0 + 1 \cdot A_1 = 0 \cdot A_0 + A_1 = A_1.$$

Hence the expression is correct.

## Truth Table

Here is the full truth table listing all combinations of  $A_0, A_1, C$  and resulting  $X$ :

$A_0$	$A_1$	$C$	$X$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

**Explanation of rows:** - Rows where  $C = 0$ :  $X = A_0$  (rows 1,3,5,7). - Rows where  $C = 1$ :  $X = A_1$  (rows 2,4,6,8).

## Sum-of-Minterms Form (optional)

If you want minterms (3 variables  $A_0, A_1, C$  ordered as  $[A_0 A_1 C]$ ),  $X = 1$  for combinations: -  $[0 1 1]$  decimal 3, -  $[1 0 0]$  decimal 4, -  $[1 1 0]$  decimal 6, -  $[1 1 1]$  decimal 7.


So one can write:

$$X = \sum m(3, 4, 6, 7),$$

which simplifies back to  $X = \overline{C}A_0 + CA_1$ .
 
## Gate-Level Implementation (diagram)


Below is a simple gate-level schematic drawn using basic TikZ shapes (no special gate library required). (Notation: rectangles labeled AND/OR/NOT are used to represent gates.)



## Implementation Steps (practical)

If you were to implement this on breadboard or in a simple digital trainer:

 1. Use one inverter (NOT) for the select line  $C$  to obtain  $\overline{C}$ .
2. Use two 2-input AND gates:
  - AND1: inputs  $\overline{C}$  and  $A_0 \rightarrow$  output  $T_0$ .
  - AND2: inputs  $C$  and  $A_1 \rightarrow$  output  $T_1$ .
3. Use one 2-input OR gate: OR inputs  $T_0, T_1 \rightarrow X$ .



## Conclusion

- The multiplexer equation  $X = \overline{C}A_0 + CA_1$  correctly implements the required selection behavior.
- The full truth table above confirms the mapping of inputs to output for all input combinations.
- The gate-level implementation uses one inverter, two ANDs and one OR (standard, minimal realization).